

LINEAR FEEDBACK SHIFT REGISTER

K. Sweta, T. John Institute of Technology

January 31, 2022

ABSTRACT

The VLSI testing is a process that takes place after chip fabrication to detect possible manufacturing defects. Imperfections in the chip fabrication may lead to manufacturing defects. Hence, testing is important. Fault detection is a technique where a fault is sensitized by applying proper test vector values at the primary inputs of the circuit so that an error is generated at a circuit node, and afterwards this error is propagated to primary output to be observed. So LFSR (Linear Feedback Shift Register) is the circuit that generates pseudorandom test patterns which will be used for testing any IC (Integrated circuit). The implementation of CMOS based LFSR circuit is used for producing pseudorandom patterns. An LFSR is a shift register that advances the signal through the register from one bit to the next most-significant bit when clocked. Two or more of the outputs are combined and given as input to the exclusive-OR gate, to form a feedback mechanism.

REFERENCE CIRCUIT DETAILS

In a LFSR, D flip flops are used to form the shift register blocks and the output of few D flip flops is given to an EX-OR gate. Whose output is fed back to the first flipflop. This is called the feedback mechanism. Linear feedback shift registers make extremely good pseudorandom pattern generators. When the outputs of the flip-flops are loaded with a seed value (anything except all 0s, which would cause the LFSR to produce all 0 patterns) and when the clock signal is applied to the LFSR, it will generate a pseudorandom pattern of 1s and 0s. The only signal necessary to generate the test patterns is the clock. A n-bit LFSR produces the maximum number of PRPG patterns possible and has a pattern count equal to $2^n - 1$, where n is the number of register elements in the LFSR. The generation of patterns is done by transition. For example, for a 4-bit LFSR there will be $2^4 - 1 = 15$ patterns generated and from 16th it will return to

its original seed value. The D flipflop used in the shift register can be designed using

REFERENCE CIRCUIT

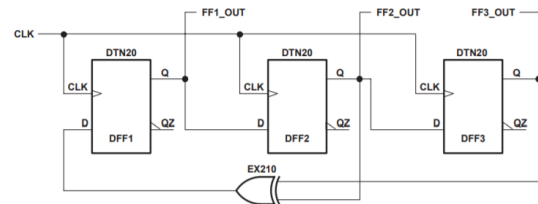


Figure 1: LFSR circuit from TEXAS instruments paper


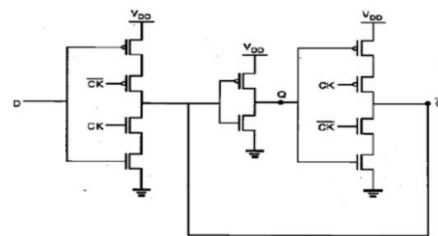


Figure 2: D flip flop, CMOS implementation.

REFERENCE WAVEFORM

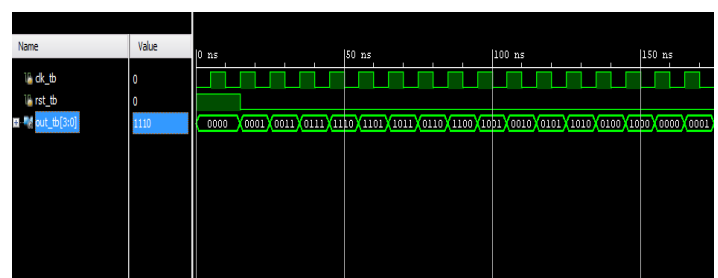

REFERENCES

- [1] "R. Saraswathi and R. Manikandan, "Design of LFSR (linear feedback shift register) for low power test pattern generator," 2017 International Conference on Networks & Advances in Computational Technologies (NetAct), 2017.
- [2] D. Datta, B. Datta and H. S. Dutta, "Design and implementation of multibit LFSR on FPGA to generate pseudorandom sequence number," 2017 Devices for Integrated Circuit (DevIC), 2017.
- [3] "What's an LFSR?", TEXAS INSTRUMENTS, December 1996.